

DÁP AN MÔN MẠCH ĐIỆN

Câu 1: α điểm
+10 mạch:

$$\begin{cases} U_a \left(\frac{1}{50} + \frac{1}{-j100} \right) - \frac{U_c}{50} = 0 \\ U_c \left[\frac{1}{(20+10j)} + \frac{1}{50} \right] - \frac{250 \angle 0^\circ}{(20+10j)} - \frac{U_a}{50} = 0,25đ \end{cases}$$

$$\begin{cases} U_a = U_{ab} = 500 \angle -53,13^\circ \text{ (V)} \\ U_c = 559,02 \angle -26,57^\circ \text{ (V)} \end{cases} \quad 0,25đ$$

Ngắn mạch:

$$I_{ng} = \frac{250 \angle 0^\circ}{20+10j+50} = 3,54 \angle -8,13^\circ \text{ (A)} \quad 0,5đ$$

$$Z_{td} = 100\sqrt{2} \angle -45^\circ \text{ (}\Omega\text{)} = 100 - 100j \text{ (}\Omega\text{)} \quad 0,25đ$$

Để công suất trên R_L đạt cực đại, điều kiện là:

$$\begin{aligned} R_L &= 100\sqrt{2} \text{ (}\Omega\text{)} \quad 0,25đ \\ I &= \frac{500 \angle -53,13^\circ}{Z_{td} + R_L} = 1,92 \angle -30,63^\circ \text{ (A)} \quad 0,25đ \end{aligned}$$


$$P_{R_L \text{ max}} = R_L \cdot I^2 = 517,54 \text{ W} \quad 0,25đ$$

Câu 2: α điểm

$$\begin{cases} U_a \left(\frac{1}{6} + \frac{1}{2} \right) - \frac{U_1}{6} - \frac{U_2}{2} = -2I_0 \\ U_1 \left(\frac{1}{6} + \frac{1}{3} \right) - \frac{U_a}{6} = I_1 \\ U_2 - U_a = 2I_2 \\ I_0 = \frac{U_1}{3} \end{cases}$$

$$\begin{cases} I_1 = \frac{5}{8} U_1 - \frac{1}{8} U_2 \\ I_2 = \frac{3}{8} U_1 + \frac{1}{8} U_2 \end{cases} \Rightarrow \begin{cases} U_1 = I_1 + I_2 \\ U_2 = -3I_1 + 5I_2 \end{cases} \quad 0,25đ$$
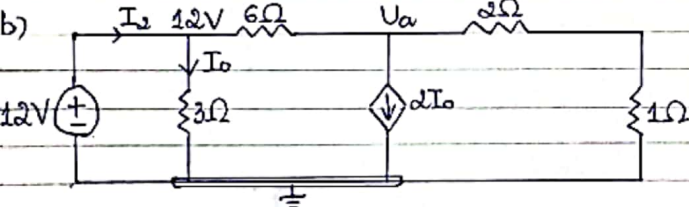
$$\Rightarrow Z = \begin{bmatrix} 1 & 1 \\ -3 & 5 \end{bmatrix} \text{ (}\Omega\text{)}$$



$$\begin{cases} U_a \left(\frac{1}{3} + \frac{1}{6} \right) - \frac{12}{6} = -2I_0 \\ I_0 = \frac{12}{3} = 4 \text{ (A)} \end{cases} \Rightarrow U_a = -12 \text{ V} \quad 0,25đ$$

$$P_{tải} = \frac{(12-U_a)^2}{6} + \frac{U_a^2}{3} + \frac{12^2}{3} = 192 \text{ W} \quad 0,25đ$$

$$P_{nguồn} = 12I_2 - U_a \cdot 2I_0 = 192 \text{ W} \quad 0,25đ$$

$$I_2 = I_0 - \left(\frac{U_a - 12}{6} \right) = 8 \text{ A} \quad 0,25đ$$

Câu 3: α điểm

$$Z_{td} = -jX_c + \frac{r \cdot 2j}{n+2j} = \frac{4n}{n^2+4} + j \left(\frac{2r^2}{n^2+4} - X_c \right) \quad 0,5đ$$


$$P = U \cdot I \Rightarrow I = 4 \text{ A} \quad 0,25đ$$

$$\frac{U}{I} = \frac{4n}{n^2+4} = \frac{1}{4} \Rightarrow \begin{cases} n = 15,75 \Omega, X_c = 1,968 \Omega \\ n = 0,254 \Omega, X_c = 0,032 \Omega \end{cases}$$

$$\frac{2r^2}{n^2+4} - X_c = 0 \quad 0,5đ \quad 0,5đ$$

ELCI140144 (NGÀY THI 14/07/2020)

Câu 4: α điểm
ĐKBD:

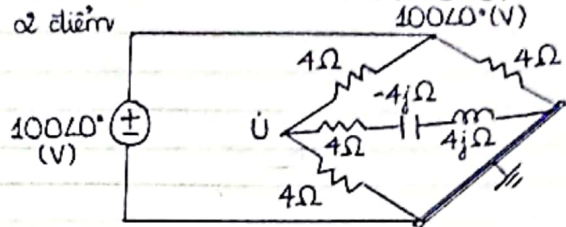


$$U \left(\frac{1}{4} + \frac{1}{4} + \frac{1}{4} \right) = \frac{100 \angle 0^\circ}{4} \Rightarrow U = \frac{100}{3} \angle 0^\circ \text{ (V)} \quad 0,25đ$$

$$I = \frac{U}{4} = \frac{25}{3} \angle 0^\circ \text{ (A)}; U_c = (-4j)I = \frac{100}{3} \angle -90^\circ \text{ (V)}$$

$$\begin{cases} i_L(t) = \frac{25}{3} \cos 8t \text{ (A)} \\ u_c(t) = \frac{100}{3} \cos(8t - 90^\circ) \text{ (V)} \end{cases} \Rightarrow \begin{cases} i_L(-0) = \frac{25}{3} \text{ A} \\ u_c(-0) = 0 \end{cases} \quad 0,25đ$$

Áp dụng định lý thevenin:
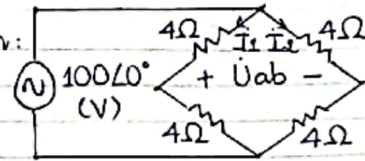
$$\begin{aligned} \text{Hở mạch: } I_1 = I_2 &= \frac{100 \angle 0^\circ}{4+4} \\ &= 12,5 \text{ A} \end{aligned}$$



$$U_{ab} = 4(I_2 - I_1) = 0 \text{ (V)} \quad 0,25đ$$

$$R_{td} = \frac{4}{2} + \frac{4}{2} = 4 \text{ (}\Omega\text{)} \quad 0,25đ$$

Mạch tương đương thevenin:

$$I = \frac{25/6}{8 + 32/p + 0,5p} = \frac{25 \cdot 3 \cdot p}{(p+8)^2} \quad 0,5đ$$

$$\Rightarrow i(t) = \frac{25}{3} e^{-2t} - \frac{200}{3} t \cdot e^{-2t} \text{ (A)} \quad 0,25đ$$


Câu 5: α điểm

$$\begin{cases} U_a \left(\frac{1}{9 + 10^4/p} + \frac{1}{1 + 10^4/p} \right) - U_1 \left(\frac{1}{9 + 10^4/p} \right) = 0 \\ U_b \left(\frac{1}{2} + \frac{1}{18} \right) - U_2 \cdot \frac{1}{18} = 0; U_a = U_b \end{cases} \quad 0,25đ$$

$$\Rightarrow W(p) = \frac{U_2}{U_1} = \frac{p + 10^4}{p + 2 \cdot 10^3} \quad 0,25đ$$

$$\begin{aligned} \text{TSG} &= 2 \cdot 10^3, 10^4; \text{ thay } p = j\omega \Rightarrow W(j\omega) = \frac{j\omega + 10^4}{j\omega + 2 \cdot 10^3} \\ 20 \lg |W(j\omega)|_{\omega=0} &= -14 \text{ dB} \end{aligned}$$
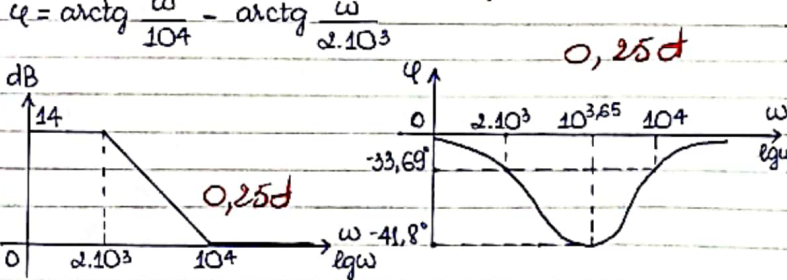
$$\varphi = \text{arctg} \frac{\omega}{10^4} - \text{arctg} \frac{\omega}{2 \cdot 10^3} \quad 0,25đ$$



$$\begin{aligned} \text{b) } u_2(t) &= 50 + 134,83 \sin(10^3 t - 20,85^\circ) \\ &\quad + 28,95 \sin(3 \cdot 10^3 t + 5,39^\circ) \text{ (V)} \end{aligned} \quad 0,5đ$$

$$\begin{aligned} U_2(\text{hđ}) &= \sqrt{50^2 + \left(\frac{134,83}{\sqrt{2}} \right)^2 + \left(\frac{28,95}{\sqrt{2}} \right)^2} \\ &= 109,58 \text{ (V)} \end{aligned} \quad 0,25đ$$