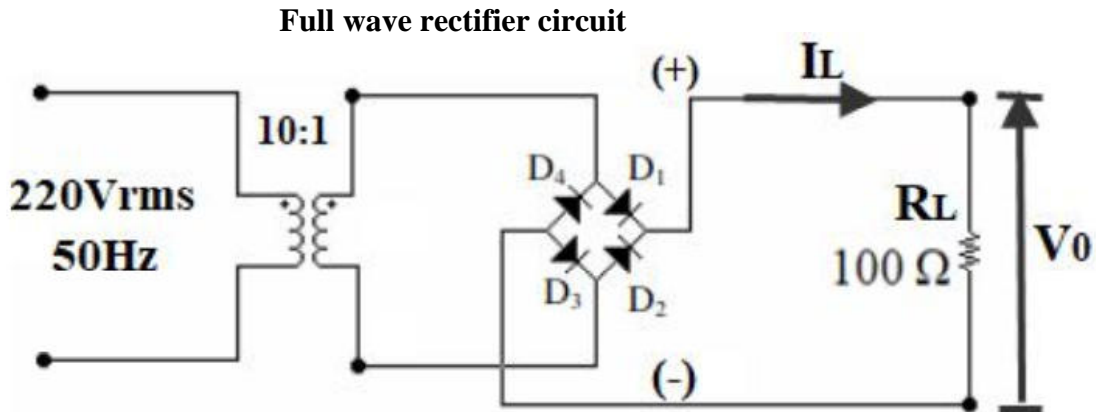


SENTENCE 1 ( 2 M )




Average output voltage is calculated by:

$$V_{0(dc)} = \frac{2 ( 22 \sqrt{2} - 1.4 )}{\pi} = 18.91 \text{ V}$$

From Ohm 's law, load current has average value as:  $I_L = 18.91 \text{ V} / 0.1 \text{ K} = \underline{189.1 \text{ mA}}$

SENTENCE 2 ( 2 M )

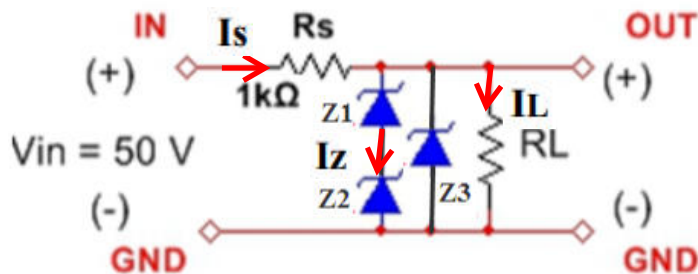

Clearly, Z3 OFF and Z1, Z2 ON at the same time.

In addition, permissible maximum current flowing through Z1 and Z2 in series is calculated as:

$$I_{Zmax} = 120 \text{ mW} / 5 = 24 \text{ mA} \text{ for ensuring reliability in service.}$$

It can be noticed that output voltage has constant amount such as:  $V_0 = 10\text{V}$

As It's known, current through resistor Rs keeps constant regardless of load resistance

In other words, it's represented as:  $I_s = ( 50 - 10 ) / 1\text{K} = 40 \text{ mA} = \text{const}$

Further more, according to Kirchhoff 's current law, it can be written as:

$$I_s = I_z + I_L = \text{const}$$

Where,  $I_z$  is current through the branch including Z1 and Z2 connected in series.

And  $I_L$  is current through load  $R_L$ .

It's easy to see that, due to  $I_s = \text{const}$ , we get the following expressions:

$$I_s = I_{zmin} + I_{Lmax} = \text{const}$$


$$I_s = I_{zmax} + I_{Lmin} = \text{const}$$

As a result, maximum load current  $I_{Lmax} = 40 \text{ mA}$ .

And minimum load current  $I_{Lmin} = 40 - 24 = 16 \text{ mA}$

Briefly, the range of load current can be depicted such as:  $16 \text{ mA} < I_L < 40 \text{ mA}$

SENTENCE 3 ( 2M )

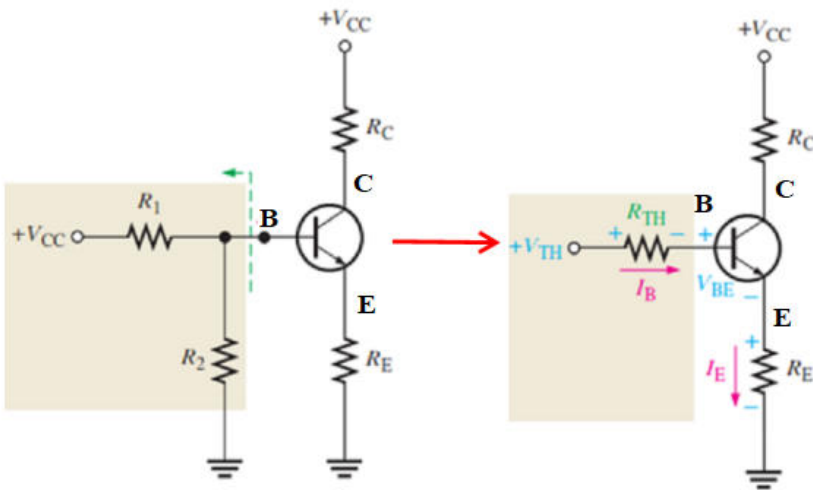

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = 5.4V$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = 6K$$

$$I_B = (5.4 - 0.7) / (6K + 10K) = 0.29mA$$


Hence,  $I_C = I_E = 29mA$

From KVL, it results in:

$$V_{CE} = V_{CC} - (R_C + R_E)I_C = -0.4V$$

It can be concluded that BJT is in saturation mode.

SENTENCE 4 ( 2M )

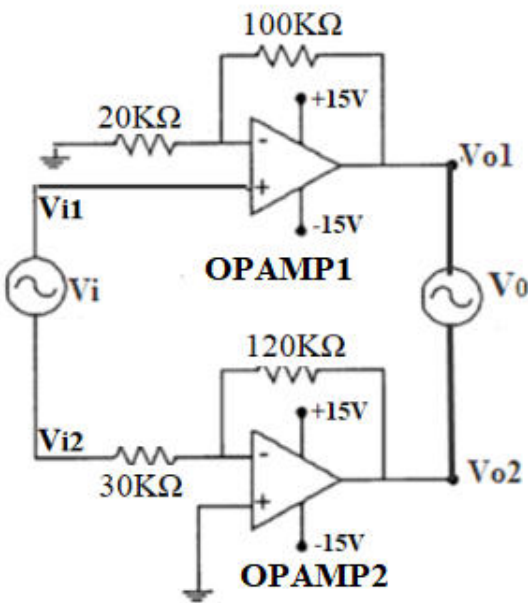

As it's given,  $V_i$  and  $V_o$  include ac and dc components.

In details,  $V_i = 0.2\exp(j30) + 0.5$

with  $V_i(ac) = 0.2\exp(j30)$  [V] and  $V_i(dc) = 0.5V$

$V_o = 4\exp(j210) + 10$

where  $V_o(ac) = 4\exp(j210) = -4\exp(j30)$  [V]

and  $V_o(dc) = 10V$

By superposition,

OPAMP 1 operating as noninverting amplifier and OPAMP 2 as inverting amplifier.

As a result,  $V_{o1} = 6V_{i1}$  and  $V_{o2} = -4V_{i2}$

Hence, we get equation systems as following

$$\begin{aligned} V_{i1} - V_{i2} &= 0.5 \\ 6V_{i1} + 4V_{i2} &= 10 \end{aligned} \quad (\text{dc quantities})$$

$$\begin{aligned} V_{i1} - V_{i2} &= 0.2\exp(j30) \\ 6V_{i1} + 4V_{i2} &= -4\exp(j30) \end{aligned} \quad (\text{ac quantities})$$

Solve with matrix of determinant, it can be described as:

$$V_{o1} = -1.92\exp(j30) + 7.2 \text{ [V]} \text{ and } V_{o2} = 2.08\exp(j30) - 2.8 \text{ [V]}$$

SENTENCE 5 ( 2M )

Output Boolean expression is determined by:  $Y = AB + \overline{BC}$

3 variable K map is represented as following:

