

PROBLEM 1 (2M)

Express the right voltage source and two right-most resistors as a Thevenin equivalent , with Thevenin voltage $20/(20+30) * (-10V) = -4V$ and Thevenin resistance $20 \Omega // 30 \Omega = 20 \times 30 / (20+30) = 12 \Omega$

According to superposition theorem , two output voltages are calculated as follows

Case 1 : $V_{IN1} = -4V$, $V_{IN2} = +5V$ (short-cuited) , OPAMP becomes inverting amplifier


Hence, $V_{OUT1} = (- 24 / 12 + 12) (-4) = + 4V$

Case 2 : $V_{IN2} = +5V$, $V_{IN1} = -4V$ (short-circuited) , OPAMP is known as noninverting amplifier

Hence , $V_{OUT2} = (1 + 24 / 12 + 12) (+5) = +10V$

Finally , $V_{OUT} = V_{OUT1} + V_{OUT2} = +14V > + 12 V$ (positive power supply)

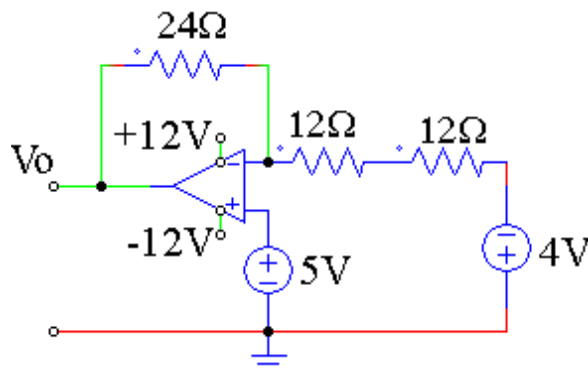It's said that OPAMP is in positive saturation and $V_{OUT} = + 12 V$



PROBLEM 2 (2M)

$I_{ZMAX} = P_{ZMAX} / V_Z = 150mW / 12 = 12,5mA$

$I_S = (36 - 12) / 1,5K = 16mA$

$I_S = I_Z + I_B = \text{const (from KCL at node B)}$

$I_{BMIN} = 16 - 12,5 = 3,5mA$


$I_{CMIN} = 100 \times 3,5mA = 0,35A$

$R_{LMAX} = 12 / 0,35 = 34,3 \Omega$

$I_{BMAX} = I_S - I_{ZMIN} = 16mA$

$I_{CMAX} = 100 \times 16mA = 1,6A$

$R_{LMIN} = 12 / 1,6 = 7,5 \Omega$

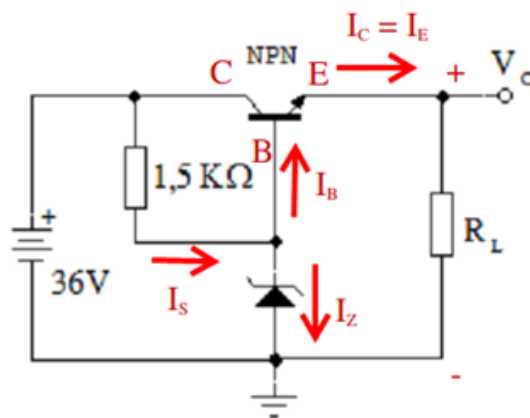

PROBLEM 3 (2M)

$I_C = I_E = 100 I_B$

$6 = 10K \cdot I_B + 0,7 + 0,1K \cdot 100I_B$

$I_B = 0,265 \text{ mA}$

$I_C = I_E = 26,5 \text{ mA}$

$V_{CE} = 36 - 1K \cdot 26,5 - 0,1K \cdot 26,5 = 6,85V$

$V_E = 0,1K \cdot 26,5mA = 2,65V$


$V_{TH} = (R_2 / R_1 + R_2) * V_{CC}$

$R_2 / (R_1 + R_2) = 6 / 36 = 1 / 6$

$R_1 * R_2 / (R_1 + R_2) = 10K \Omega$

$R_1 = 60K \Omega$


$R_2 = 12K \Omega$

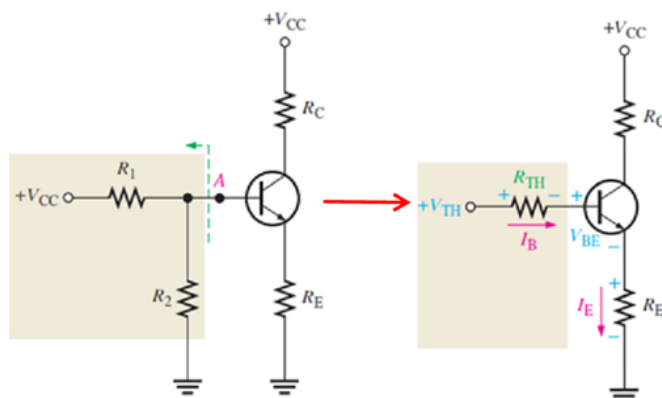

PROBLEM 4 (2M)

$$Y = \bar{A} \bar{B} X + X \bar{B} \bar{C} = 000 + 001 + 000 + 100$$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

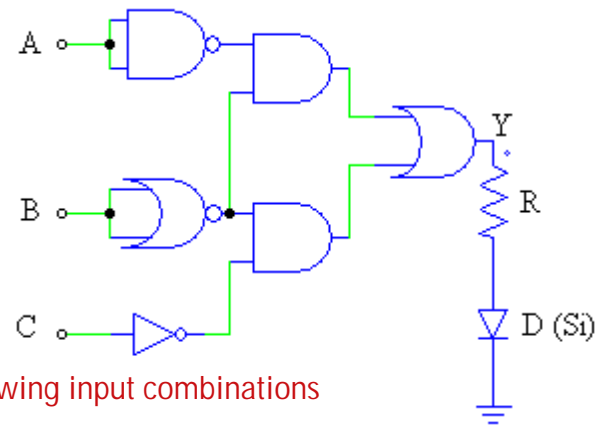

Diode ON in one of three following input combinations such as 000 , 001 , 100 .

$$R = (5 - 0.7) / 2\text{mA} = \underline{2,15 \text{ K}\Omega}$$

PROBLEM 5 (2M)

OPAMP 1 given as $A_{v1} = +6$ (noninverting amp)

Hence , $V_{o1} = (+6) * 0,5 \sin \omega t$ [V]

$$V_{o1} = 3 \sin \omega t$$
 [V]

$$V_{o2} = -9 \sin \omega t$$
 [V]

OPAMP 2 known as inverting amp

Hence , $A_{v2} = - 9 / 3 = - 3$

The total voltage gain determined by

$$A_v = (+6) (-3) = -18$$

$$R = 4,7\text{K}\Omega * 3 = 14,1\text{K}\Omega$$

