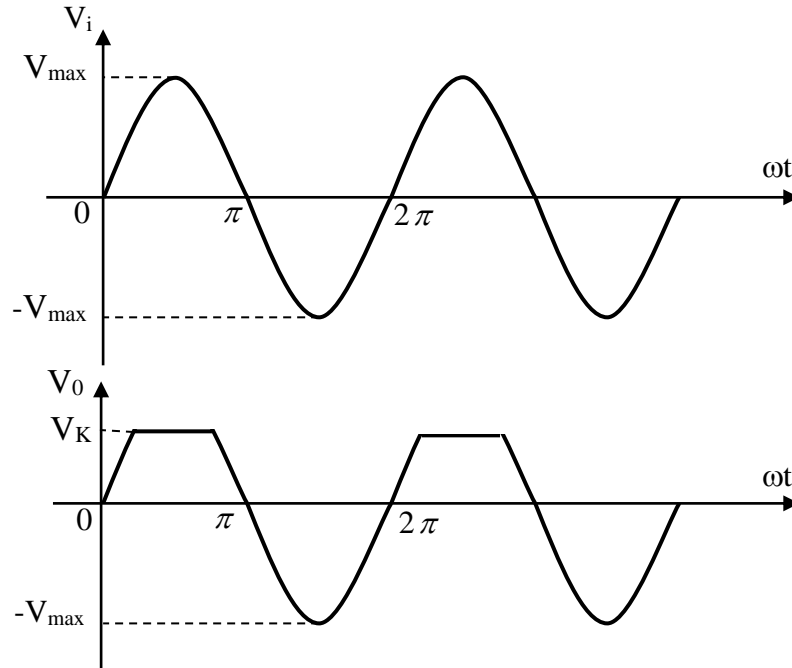


CÂU 1: (2đ)


A. (1đ)

$V_{max}=10V, V_k=4V$




Dạng sóng vào, ra của mạch xén mức trên.

b. (1đ)

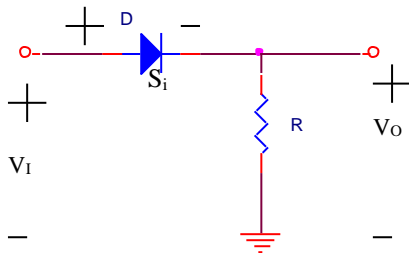

$V_m=12V$
 $V_{omax}=11,3V$

$V_{ODC}=3.6V, I_{ODC}=0,03A$

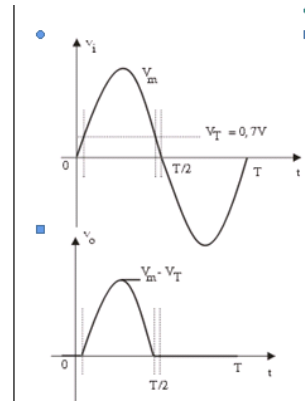

CÂU 2: (3đ)

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{(15 - 0,7)V}{680k\Omega + 101(1k\Omega)} = \frac{14,3V}{781k\Omega} = 0,018mA$$

$$I_C = \beta I_B = 100(0,018) = 1,83mA$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E) = 18V - 1,83mA(3,9 + 1k\Omega) = 6.03V$$

A. Q (1,83mA, 6,03V), BJT hoạt động khuếch đại (1.5đ)

b. Phương trình DCLL : $I_C = -0.2V_{CE} + 3,06$ (mA)

$V_E = 1,83V$

$V_C = 7,86V$ (1đ)


c. $R_B = 834K\Omega$ chọn $R_B = 820K\Omega$ (0.5đ)

Câu 3: (2đ)

(1đ)

Input			Out put
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = \overline{\overline{A}}\overline{B}C + \overline{A}\overline{B}\overline{C} + A\overline{\overline{B}}\overline{C} + ABC \quad (1đ)$$

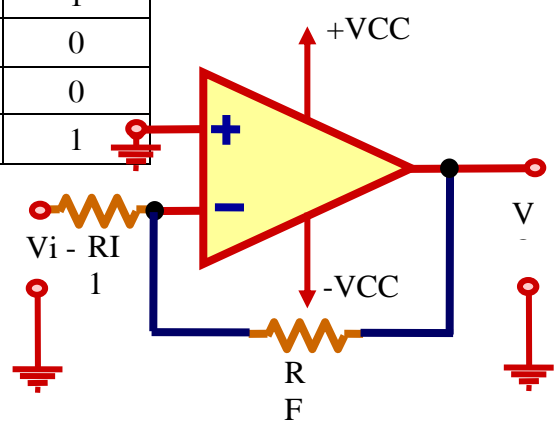

Câu 4: (2đ)

(0.5đ)

a. $A_v = -10$, $V_o = 1\sin 1000t$ (V) (1đ)

b. $R_F = 80 K\Omega$ (0.5đ)

Câu 5: (1đ)

+8V, -12V, +15V (0.5đ), (1,25V đến 37V) (0.5đ)